

Practical Scan for ASIC Designers

Anand J. Bariya

Testing Integrated Circuits


- After manufacture, chips are tested to check that they are free of manufacturing defects
 - testing is done on Automated Test Equipment (ATE), a.k.a. “testers”
 - signals are sent through primary inputs, and primary outputs checked for expected values
 - cannot probe internal nodes
 - there can be millions of internal nodes: defect on any one can cause a chip to fail

- An IC is tested multiple times before being shipped to customer:
 1. while still on the wafer, before die are cut (“die sort”): probe card
 - detect & discard devices that have defects due to wafer processing
 2. after packaging (“final test”): load board
 - detect & discard devices that have defects introduced during packaging (a.k.a. “assembly”)
 3. after “burn in”:
 - detect & discard “marginal” devices that fail after going through a stress treatment
 - would otherwise fail early in use (“infant mortality”)

Detecting Defects

- An IC is considered defective if any node in the circuit has a defect (“fault”)
 - checking for a defect on every node of the IC ensures the IC is exhaustively tested
 - difficult to guarantee exhaustive testing with direct functional vectors; also test time can get very large
- “fault model”: indicates how a fault affects a node
 - Cannot determine how to detect a faulty node without a fault model
- “stuck-at” fault model is most common:
 - Assume fault at a node causes it to be stuck to VDD (“stuck-at-1”) or to GND (“stuck-at-0”)
 - Stuck-at fault can be detected by simply trying to toggle the node (from 0 to 1, and 1 to 0) and observing if the toggling happens
 - Many defects that do not strictly result in nodes being stuck at 0 or 1 also end up being detected by tests based on the “stuck-at” fault model

 Detection of Stuck-At Faults in Combinational Logic




Controllability and Observability

- Controllability: ability to apply a desired logic value to a node by applying logic values to one or more primary inputs (PIs)
- Observability: ability to deduce the logic value at a node by checking the logic values at one or more primary outputs (POs)
- Necessary condition to test combinational logic: all inputs should be controllable and outputs observable
 - Condition is obviously satisfied if all inputs and outputs are primary


Detecting Stuck-At Faults in Sequential Circuits

 - Inputs to combinational logic may come from flip-flops, and outputs may go to flip-flops:




- If FFs at inputs are controllable, and FFs at outputs are observable, combinational logic in sequential circuit can be tested
- Circuit above satisfies this condition because:
 - FFs A, B & C: directly connected to PIs, therefore controllable
 - FF D: directly connected to PO, therefore observable

 Detecting Faults in Deeply Pipelined Sequential Logic



- Flip-flops A, B & C: difficult to control
 - inputs come from other FFs thru combo logic
 - many pipeline stages between primary inputs & FFs
- Flip-flop D: difficult to observe
 - lot of combo logic and pipeline stages between FF and primary outputs

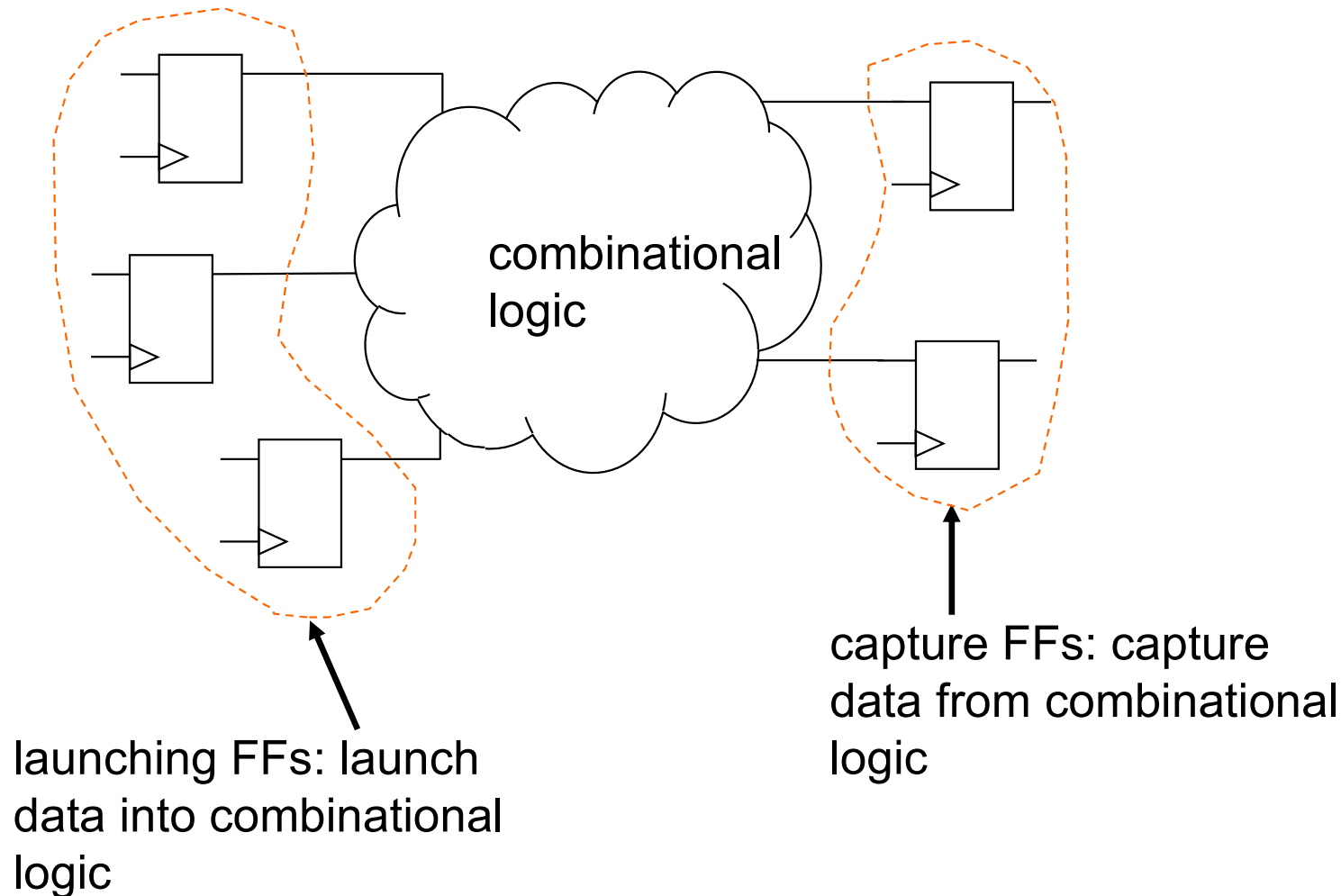
Sequential Circuit as seen from the Point of View of Test:



FFs provide inputs to, and capture outputs from, combinational logic

Testing Sequential Circuits

 
- Typical flip-flop will both launch data into combo logic, and capture data from combo logic:



these are capture FFs for combo logic on left, and launch FFs for combo logic on right

Sequential Circuit Tested with Scan

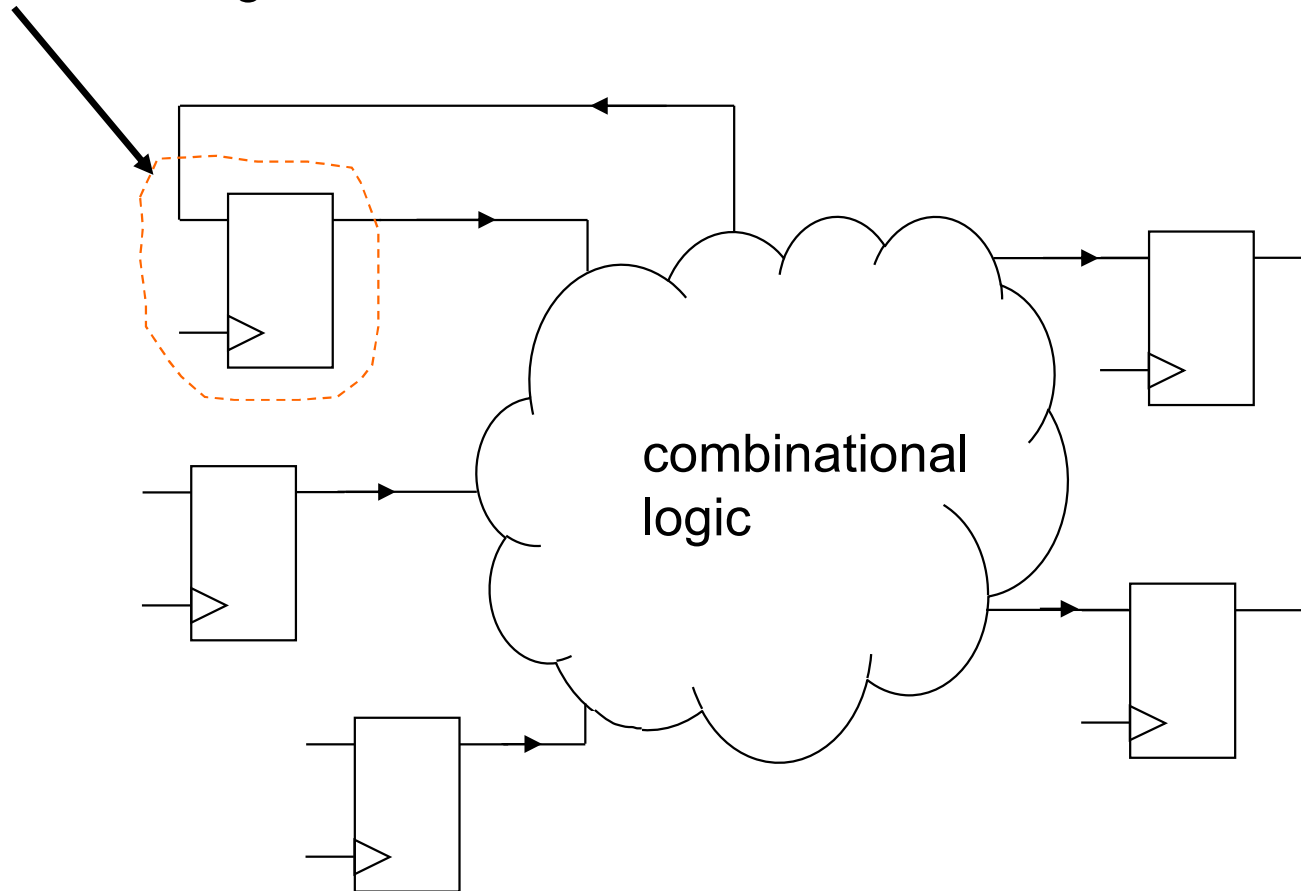- A flip-flop may launch into, and capture from, the same “cloud” of combinational logic



Design For Test (DFT) & Scan


- DFT: the inclusion of circuits or circuit elements that play no role in the functionality of a chip, but exist only to enable testing of the chip
- Scan is one among many DFT techniques
 - Used for comprehensive testing of sequential logic (logic consisting of flip-flops and combinational gates)
 - “Comprehensive” \Rightarrow large fraction of internal nodes (ideally all) are tested

Basic Idea of Scan

 
- 1) Load all flip-flops with known values
- 2) Launch these values into combinational logic
- 3) Check if values in capturing FFs are expected values
 - if not, die is defective

Scan Chains

- To load FFs with known values for test, bypass combinational logic




Original Logic

 

Mux insertion for
combinational logic bypass


Scan Chains

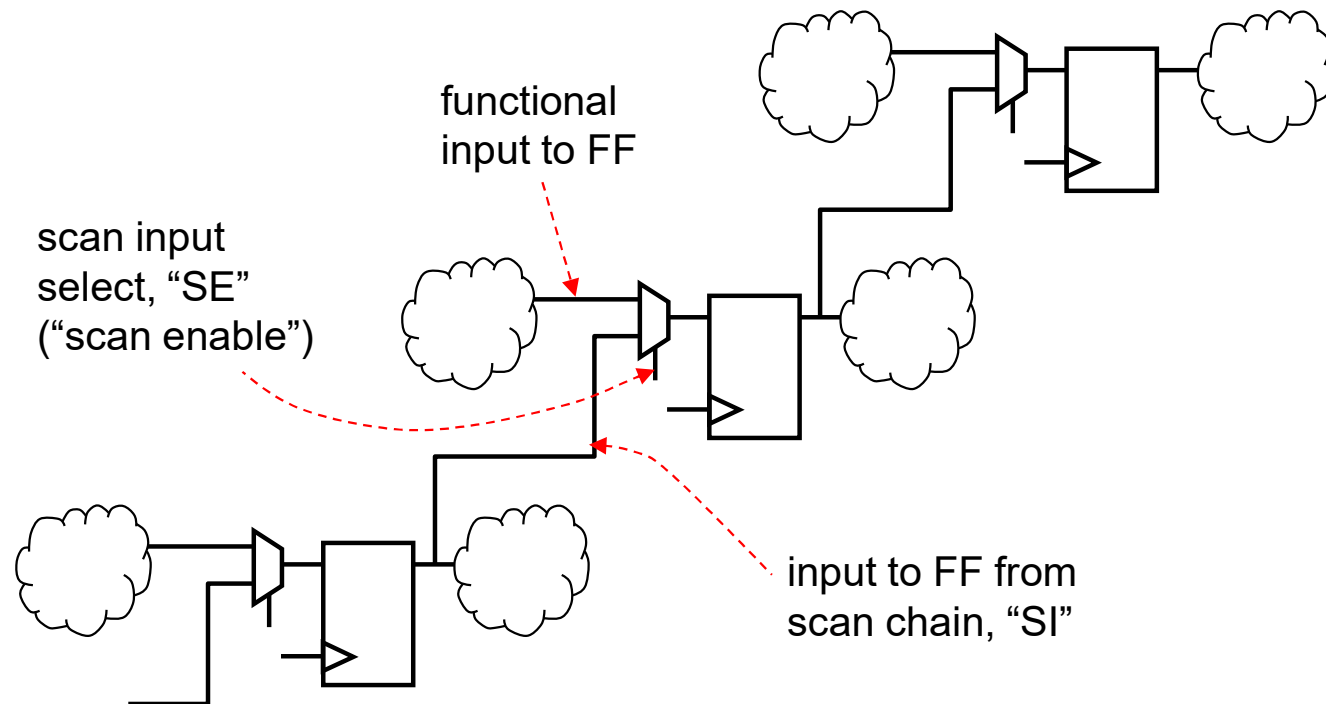- String FFs together through the combinational logic bypass to form “scan chains”



Scan Chains

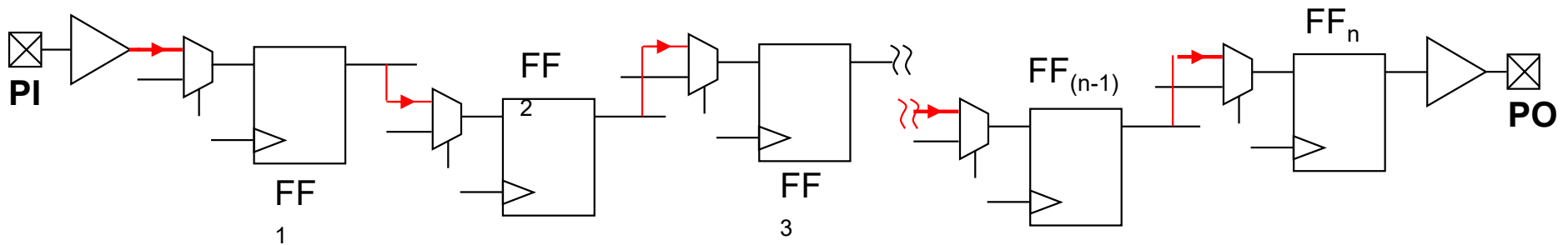
- First FF in scan chain connected to primary input (PI)
- Last FF in scan chain connected to primary output (PO)



Scan chain of length “n”

Scan Shift

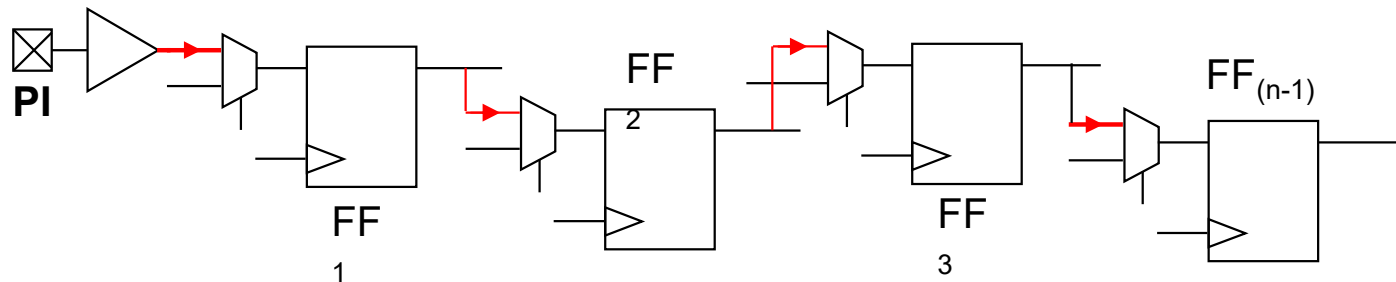- For scan chain of length “n”, all FFs can be set to desired values over “n” clock cycles
 - values fed to scan chain from PI
 - SE = 1 throughout




Scan Chains

- To load FFs with known values for test, bypass combinational logic and pipeline stages
- String flip-flops into “scan chains”, and shift values in sequentially from a primary input
 - first flip-flop in scan chain connected to primary input
 - last flip-flop in scan chain connected to primary output
 - for a scan chain with “n” flip-flops, all flip-flops will get loaded in “n” clock cycles

Scan Chains

 - Add two-input mux just before FF D-input to enable construction of a scan chain:




Mux selects of all scan muxes connected together: signal called “scan enable” or, more correctly, “shift enable” (SE)

Basics of Scan

- Scan testing involves the following steps:
 - a) shift in: load FFs with pre-determined values
 - takes “n” clock cycles for a chain of length “n”
 - SE = 1
 - b) capture: drive shifted in values through combinational logic
 - takes a single clock cycle
 - SE = 0
 - c) shift out: observe values captured in FFs
 - takes “n” clock cycles for a chain of length “n”
 - SE = 1
- Steps (a) and (c) can be combined \Rightarrow scan involves two modes:
 - i. shift (steps “a” & “c”)
 - ii. capture (step “b”)


Scan Chains

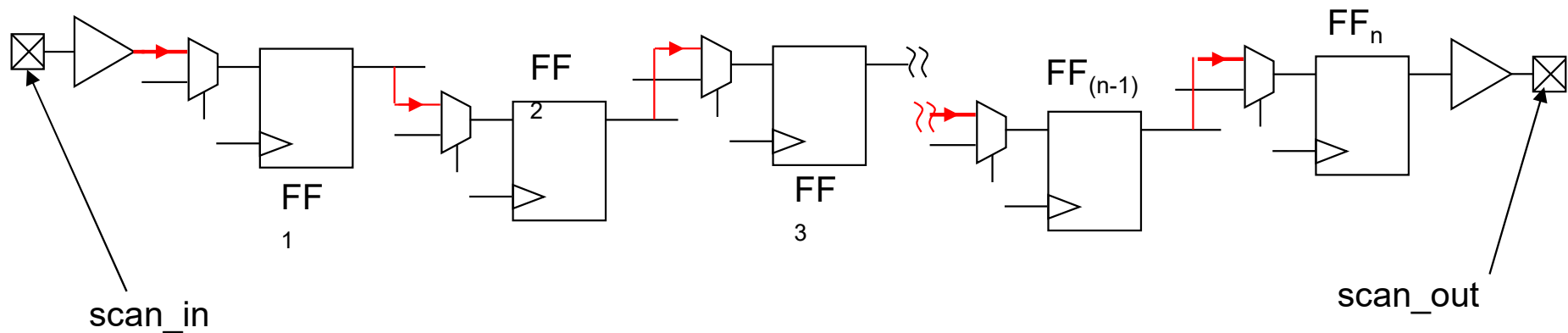- Order of flip-flops in scan chain can be completely arbitrary
 - Adjacent FFs in scan chain may drive data into same or different combinational logic
- Data enters first FF in a scan chain from a primary input and leaves last FF in scan chain from a primary output




Capture Mode

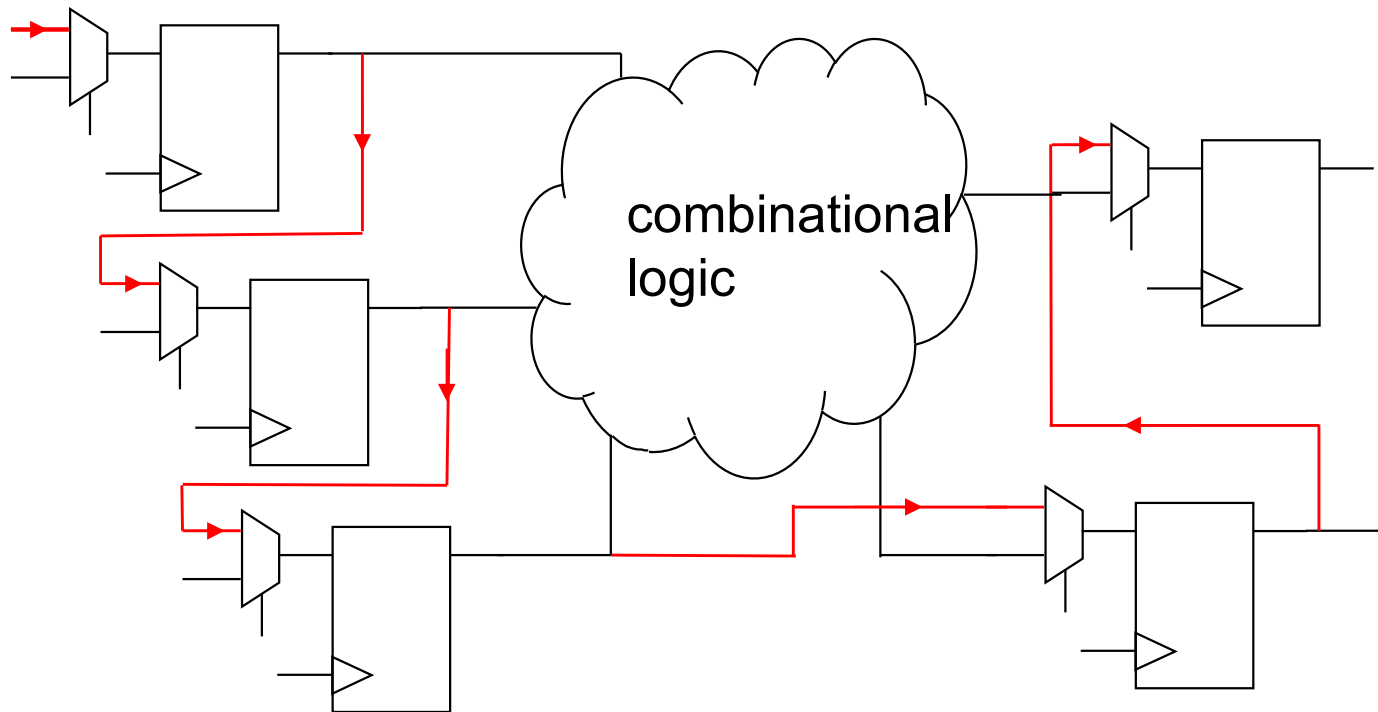- In capture mode, flip-flops drive data through, and capture data from, combinational logic



Making a Design Scannable

 
- A design is made “scannable” by the addition of a two-input mux in front of every flip-flop



- SE = “shift enable” signal
 - 1 in shift mode, 0 otherwise
- SI = scan input: input from previous FF in scan chain
 - or from “scan_in” port for first FF in scan chain
- D = functional input (comes from combinational logic)
- Note SE = 0 in both functional mode and scan capture mode

Integrated Scan Flip-flops

 - Most standard cell libraries include D flip-flops with built-in scan mux:



Value of SE in different modes

Functional mode	Scan Mode	
	Shift	Capture
0	1	0

Cost of Scan

- Both a delay penalty and an area penalty is incurred as a result of scan
 - Scan FF has higher setup time and area

Example: A flip-flop from a 40nm standard cell library




FF type	Timing (ps)		Area (μm^2)	area increase
	Setup	Hold		
Plain FF	22	6	5.3	
Scan FF	65	-30	6.5	23%

- Scan FF typically has better hold characteristics due to delay of built-in mux

Multiple Scan Chains

- More than one scan chain can be created:
 - each scan chain has its own scan_in and scan_out ports
 - SE is common for all scan chains
 - more scan chains \Rightarrow shorter scan chains \Rightarrow fewer clock cycles needed to scan in values into all FFs
 - number of scan chains usually limited by number of primary ports available for scan in & scan out, or sometimes limitation of tester

Multiple Scan Chains

 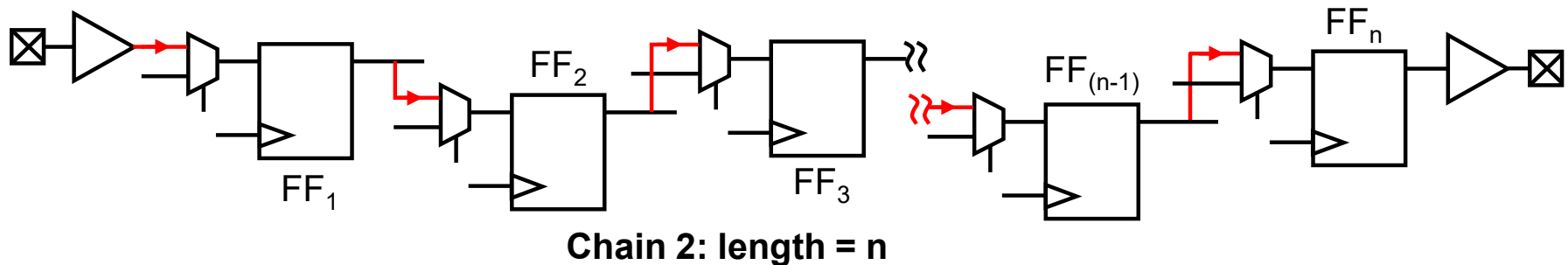 

- No. of clock periods for shift = max chain length = $\max(m, n, p)$
- With single chain, no. of clock periods for shift = length of single scan chain = $m+n+p$

Automatic Test Pattern Generation


- ATPG determines:
 - a) what values to load into every flip-flop in scan chain during shift
 - b) what is the expected value in flip-flops after capture
 - c) multiple shift-capture cycles to get coverage on all nodes

Scan Chain Balancing: Optimizing Multiple Scan Chains

- N_{shift} = no. of clock periods needed for full shift operation = max chain length
- To minimize N_{shift} , minimize max chain length
- Max chain length is minimum if all scan chains are of equal length
- Equalizing scan chain length is called “scan chain balancing”


Port Sharing

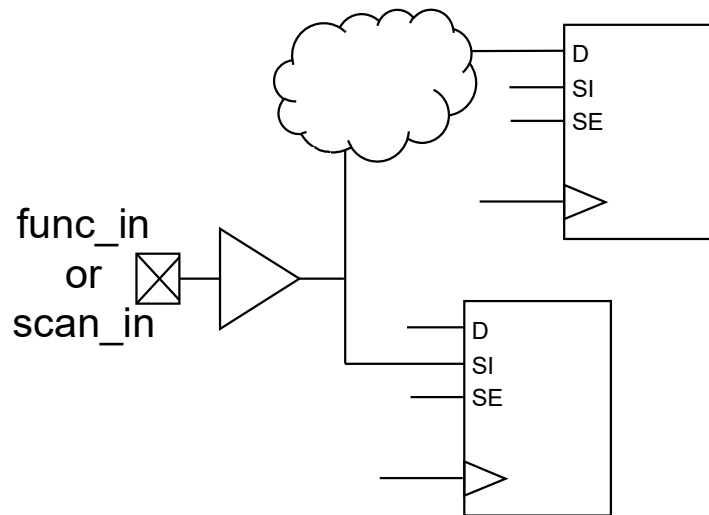- scan_in & scan_out ports need not be dedicated
 - can share functional ports



Input sharing

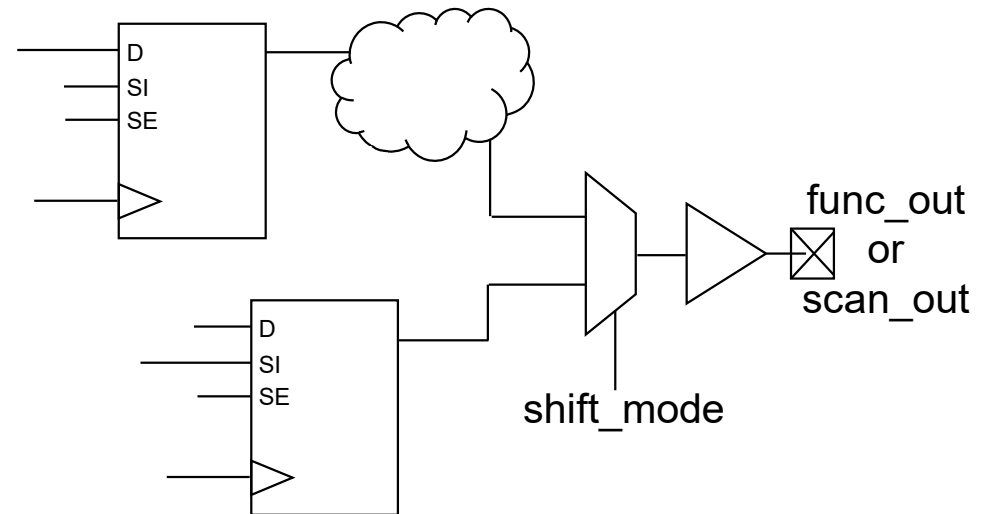- Delay through receiver increases because of increased load





Output sharing

- Delay through mux adds to output delay


Port Sharing

  - Could use bidirectional I/Os for inputs & outputs to reduce impact of port sharing on timing




Scan Clocking

 - FFs in the same scan chain can have different clock sources
 - happens if the FFs are in different clock domains in functional mode




Scan Clocking

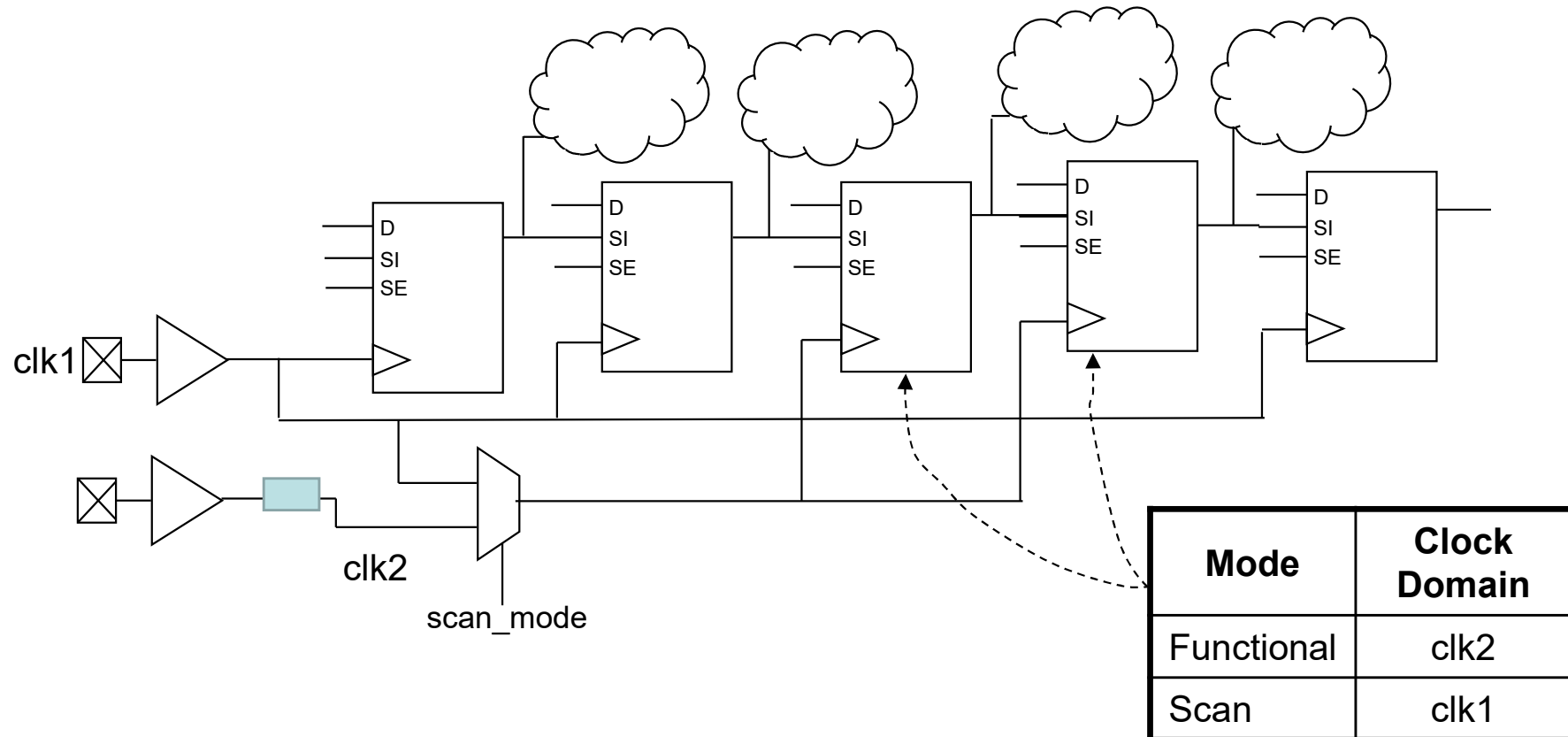- FFs can be made to have same clock in scan mode
 - requires insertion of muxes in clock paths




Shift Mode Timing

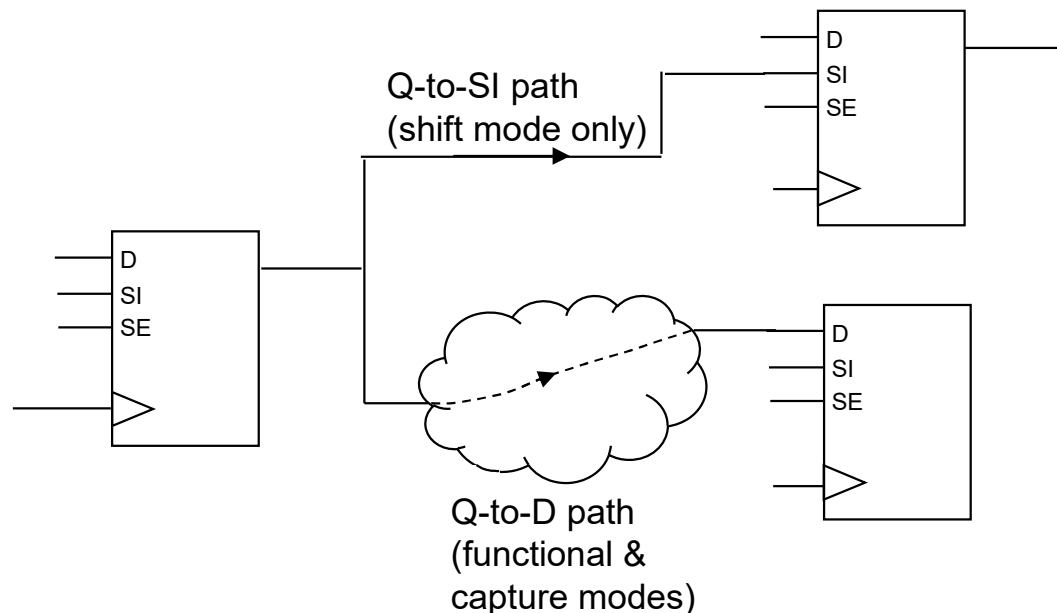- Shift can occur at slow clock speed \Rightarrow no setup violations
- Hold violations can occur during shift
 - no combinational logic on “Q-to-SI” paths \Rightarrow data goes fast from Q to SI




Shift-Mode Hold Violations Due to Clock Skew

 - clock skew between adjacent FFs in scan chain can lead to hold violations
 - skew can be particularly high if adjacent FFs are on different clock trees




Delay Insertion for Hold Avoidance

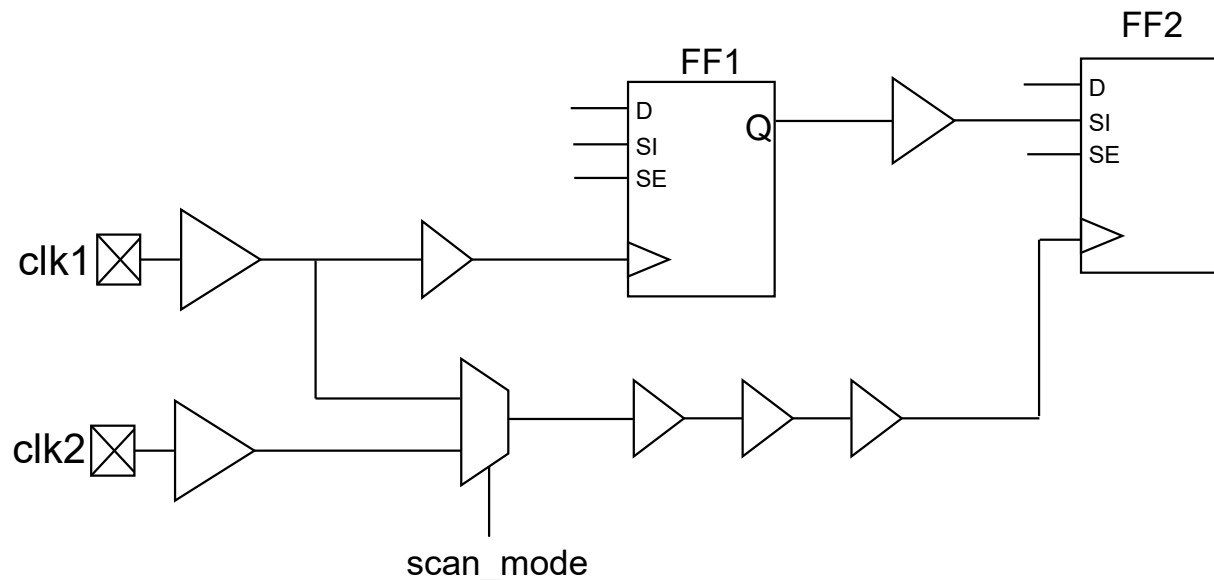- During scan stitching, blindly add large delay to Q-to-SI path when adjacent FFs are on different clock tree
 - kill the possibility of hold violation
 - setup is not a concern due to low frequency in shift mode





Lock-Up Latches as Delay Elements

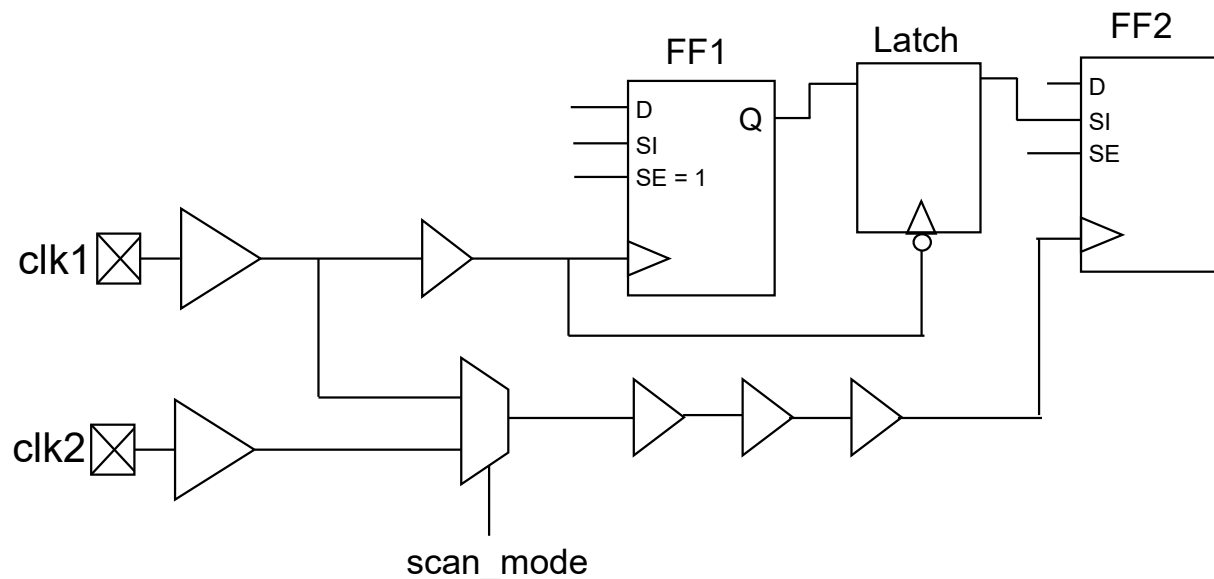- A level-sensitive latch is the most effective delay element
 - will add delay of half clock cycle (for 50% duty-cycle clock)




How a Lock-up Latch Works

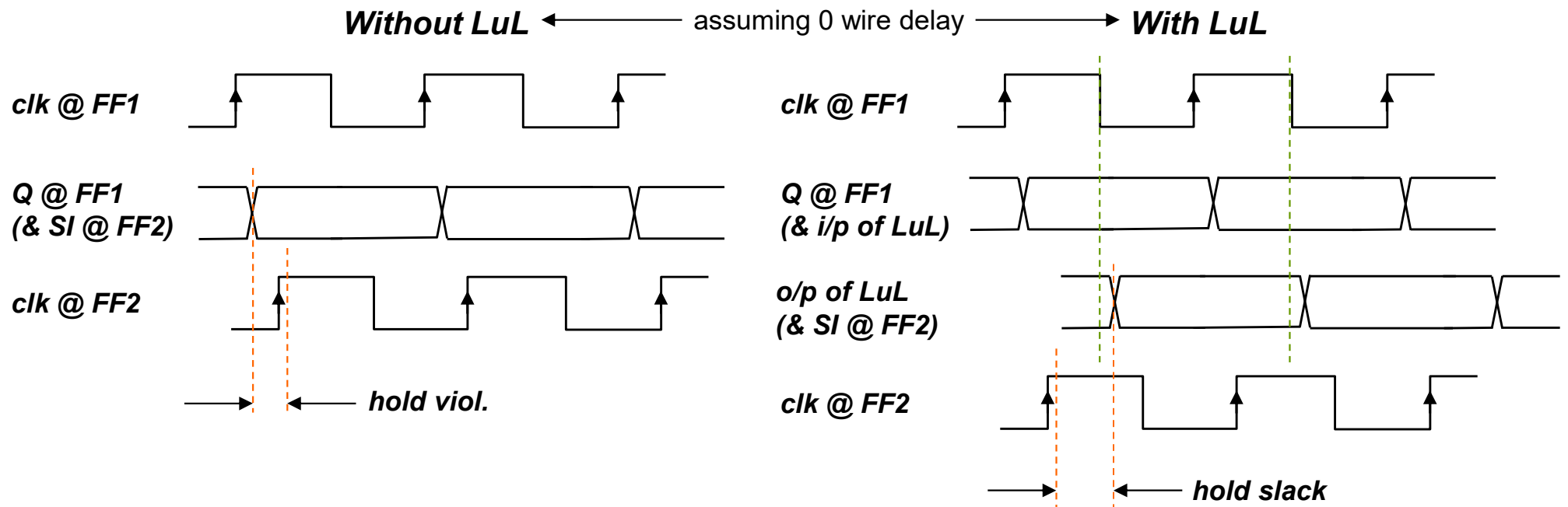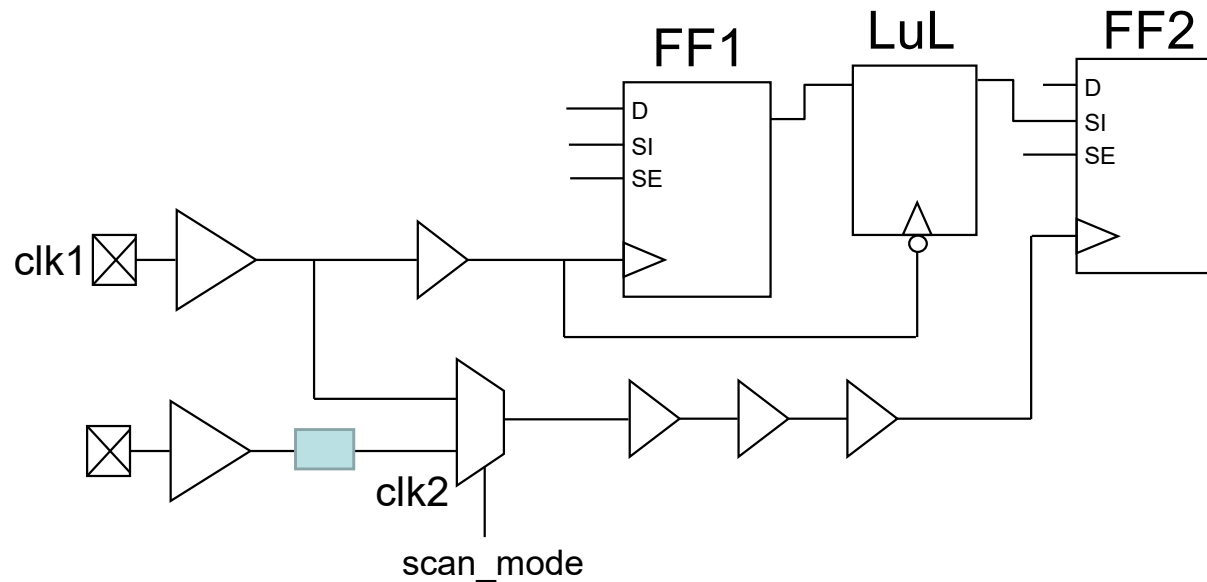


Type & Connectivity of LuL

 - “Clock” of LuL must be connected to clock of upstream FF, not downstream FF
- Must ensure right “clock polarity” of LuL:



 
**+ve edge triggered upstream FF
⇒ use “active low” LuL**



**-ve edge triggered upstream FF
⇒ use “active high” LuL**

Timing in Capture Mode

 
- Most functional-mode timing paths will also exist in scan capture mode
 - paths to/from bypassed macros exist in functional mode but not in scan capture mode
 - conversely, paths through scan bypass logic exist in scan capture mode but not in functional mode



- no false paths in scan capture mode
 - FPs in functional mode are not FPs in scan capture mode
- no multicycle paths in scan capture mode
- because clock freq. in scan mode typically much lower than in functional mode, both of the above conditions are usually okay


Cross Clock-Domain Paths in Capture Mode

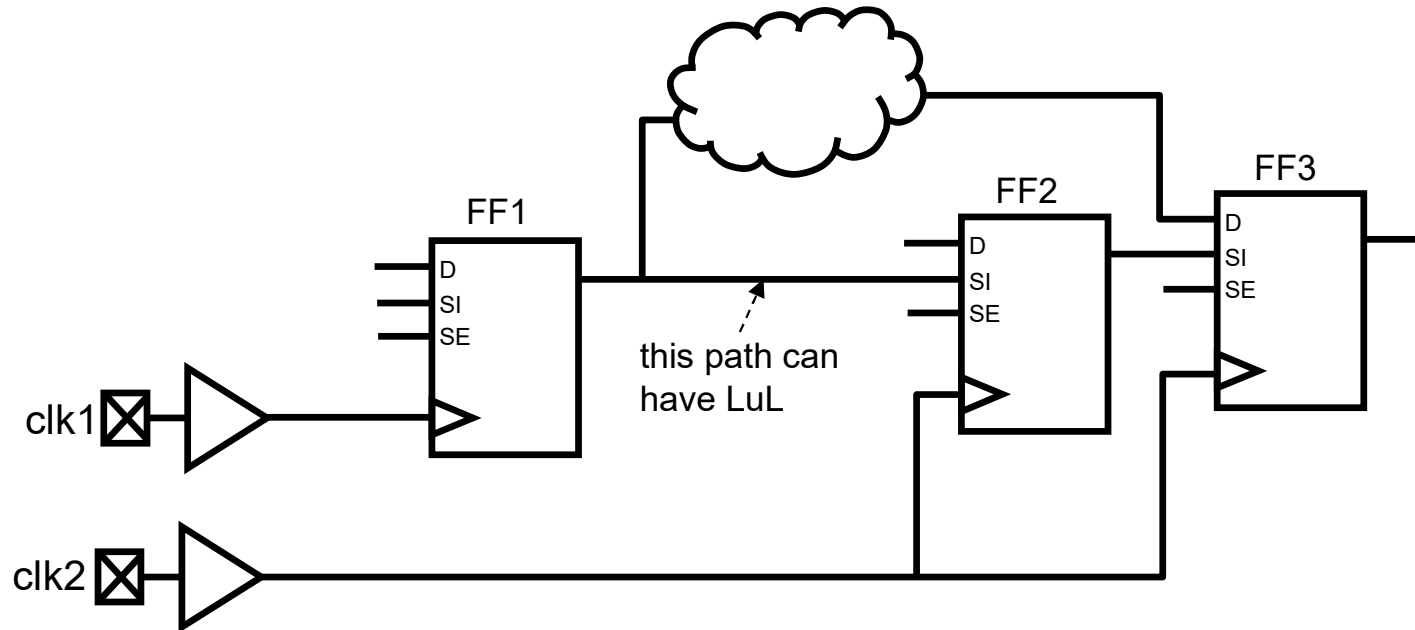- In functional mode, paths between asynchronous clock domains are false. Same paths are synchronous, and not false paths, in scan capture mode
 - all clocks have same frequency in scan mode: no asynchronous paths





- clk1, clk2 asynchronous in functional mode \Rightarrow false path between FF1 & FF3
- clk1, clk2 synchronous in scan mode
 - must meet setup and hold timing between FF1 and FF3

Cross Clock-Domain Paths in Capture Mode

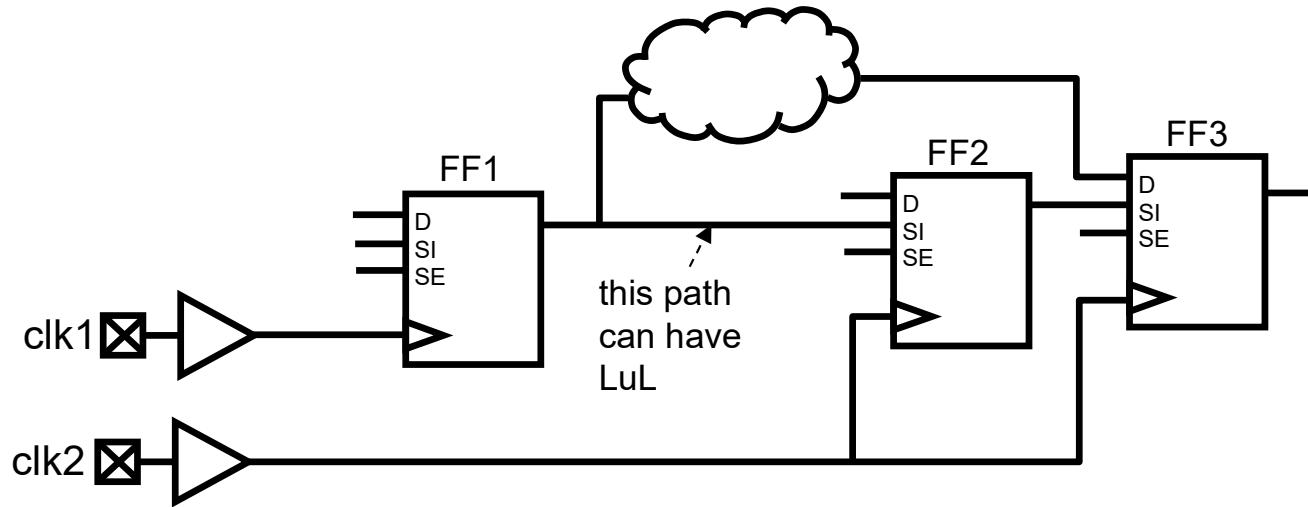


 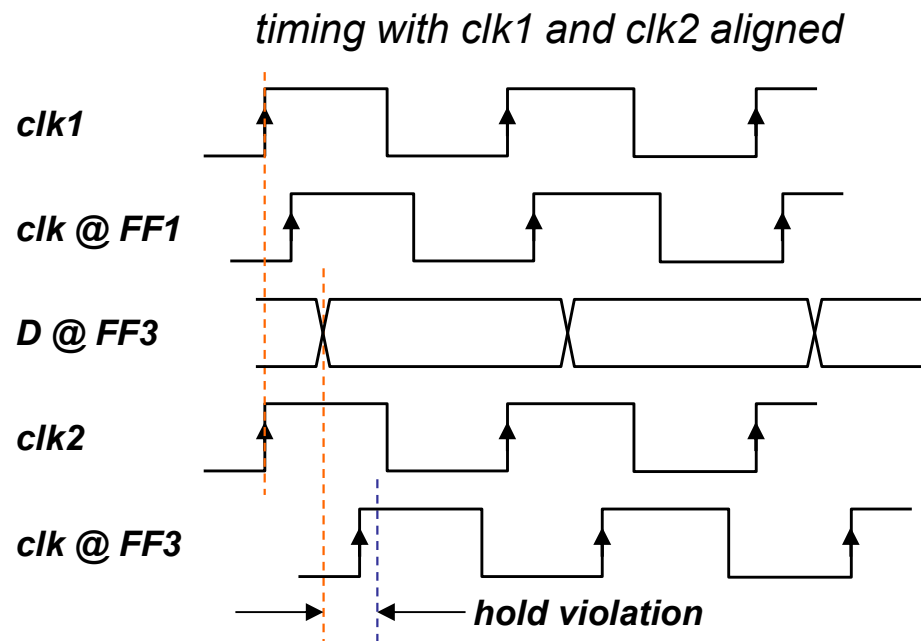clk1, clk2 separate clocks in scan mode \Rightarrow can fix hold violations by “source latency adjustment” on tester:



Cross Clock-Domain Paths in Capture Mode

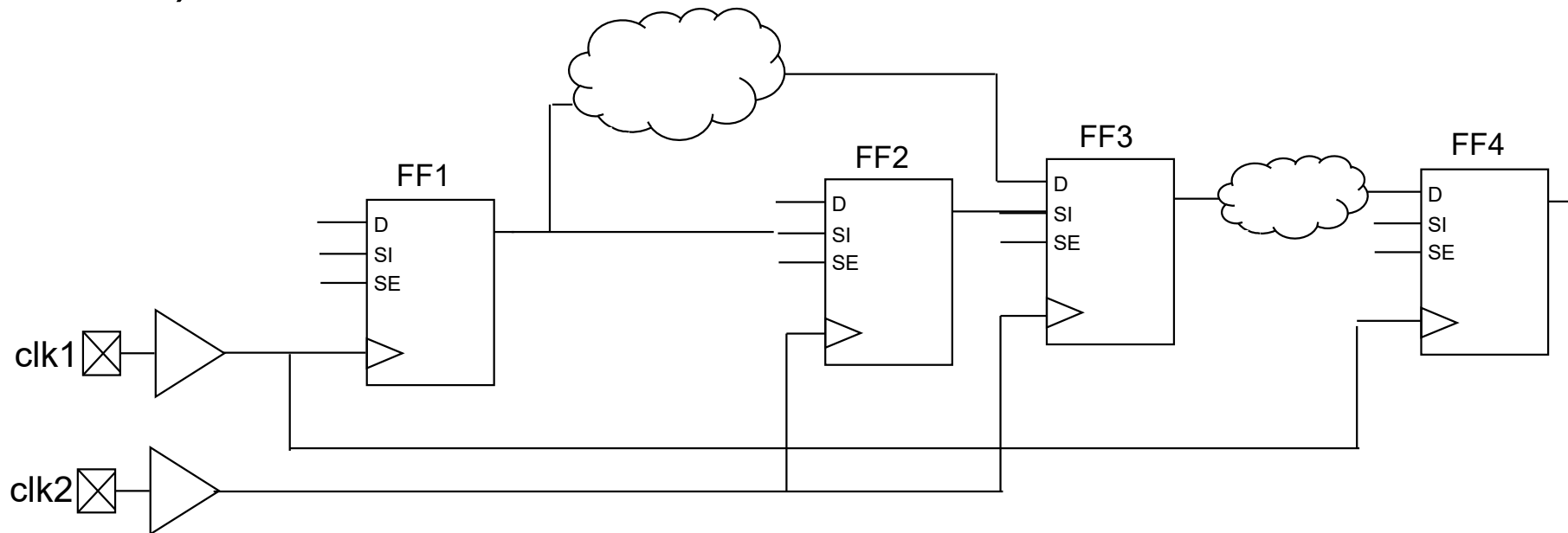
- Adjusting clock waveforms on tester will not work if there are violations in both directions (clk1-to-clk2 *and* clk2-to-clk1)



- Hold viols. in FF1-to-FF3 path *and* FF3-to-FF4 path \Rightarrow fixing one by adjusting clk1 & clk2 waveforms will worsen the other

Cross Clock-Domain Paths in Capture Mode

 
- clk2 bypassed by clk1 in scan mode \Rightarrow would need to add delay into data path between FF1 and FF3 to fix hold violation




- can affect timing in functional mode
- when possible, keep FFs in different clock domains on separate, independent clocks in scan mode

Clock Controllability

 - Clocks to all FFs in scan chains must be controllable during scan
 - Cannot use internally generated clock sources (e.g., PLLs) since tester cannot control their waveform: **internal clock sources must be bypassed in scan mode**



 $\text{clk} = \text{scan_mode} ? \text{clk_in} : \text{ckout}$




$\text{clk} = \text{scan_mode} ? \text{ref_clk} : \text{ckout}$


 
Examples of PLL bypassing in scan mode

Clock Controllability: Clock Dividers

- Clock dividers should be bypassed
 - Phase of divided clock depends on initial state of divider output \Rightarrow cannot have direct controllability of divided clock



Divide-by-2 clock divider

  

Scan-Mode Control Signals

- `shift_enable`: asserted only during shift operation (deasserted in capture)
 - connected to the “SE” pins of scannable FFs
- `scan_mode`:
 - kept asserted during entire scan operation (shift + capture)
 - deasserted in normal functional mode
 - used for “mux select” of scan-mode bypass muxes (e.g. for clocks and resets)
 - may not be needed if there are no scan-mode bypass muxes


Scan-Mode Control Signals

Signal	Mode		
	Functional	Scan	
		Shift	Capture
shift_enable	0	1	0
scan_mode	0	1	1

ATPG

- With scan chains stitched up, an ATPG tool generates scan patterns that primarily contain:
 - the sequence of 1's and 0's shifted into scan chains
 - the expected sequence of 1's and 0's shifted out of scan chains
 - clock input waveforms
 - logic levels of scan-mode control signals (scan_mode, shift_enable)
- Input to the tool is gate-level netlist
 - Tool identifies and understands combinational logic between FFs
 - Tool determines what values to drive through the logic to catch faults on as many internal nodes as possible
 - Values to be driven through combinational logic are loaded onto launching flip-flops in shift cycle

 Coverage of Combinational Logic near I/Os




- scan_in, scan_out: “scan” input and output
- in1, out1: “non-scan” input and output

During capture:

- data is driven in from in1 to get coverage in comb. logic “A”
 - data is observed at out1 to get coverage in comb. logic “B”
- ⇒ Patterns generated by ATPG tool will include input values on “non-scan” inputs, and expected values on “non-scan” outputs

 Problem of Embedded Sequential Macros

- Large embedded circuits blocks, sequential in nature (e.g. memories), have “shadow combinational logic” which can escape scan coverage




- A, B: shadow combinational logic of the macro
 - outputs of A not captured in a scannable FF
 - inputs of B are not controllable during scan

⇒ no scan coverage of A & B

Getting Coverage on Shadow Logic

- Two approaches:
 1. Add capture/control FFs
 2. Macro bypass


Adding Observe/Control FFs

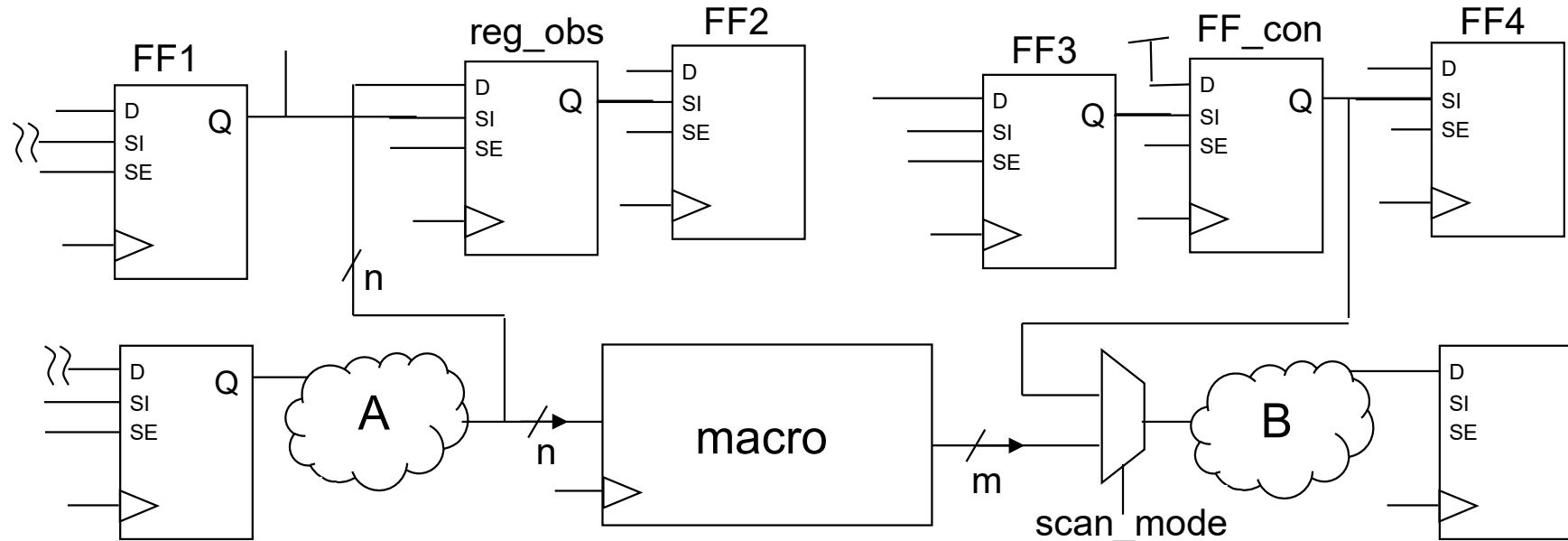

- FF1, FF2, FF3, FF4: existing functional FFs
- reg_obs: capture FFs (inserted only for test)
 - Capture outputs of “A” (at “D” pins)
 - Q’s go only to SI pins (of next FFs in scan chain) and not to any D pins: no functional role
- FF_con: control FFs (inserted only for test)
 - Drive data through “B” in scan mode
 - No functional inputs (“D” pins can be tied high or low)
 - Q’s go only to SI pins (of next FFs in scan chain) and not to any D pins: no functional role

Reducing Count of Inserted FFs

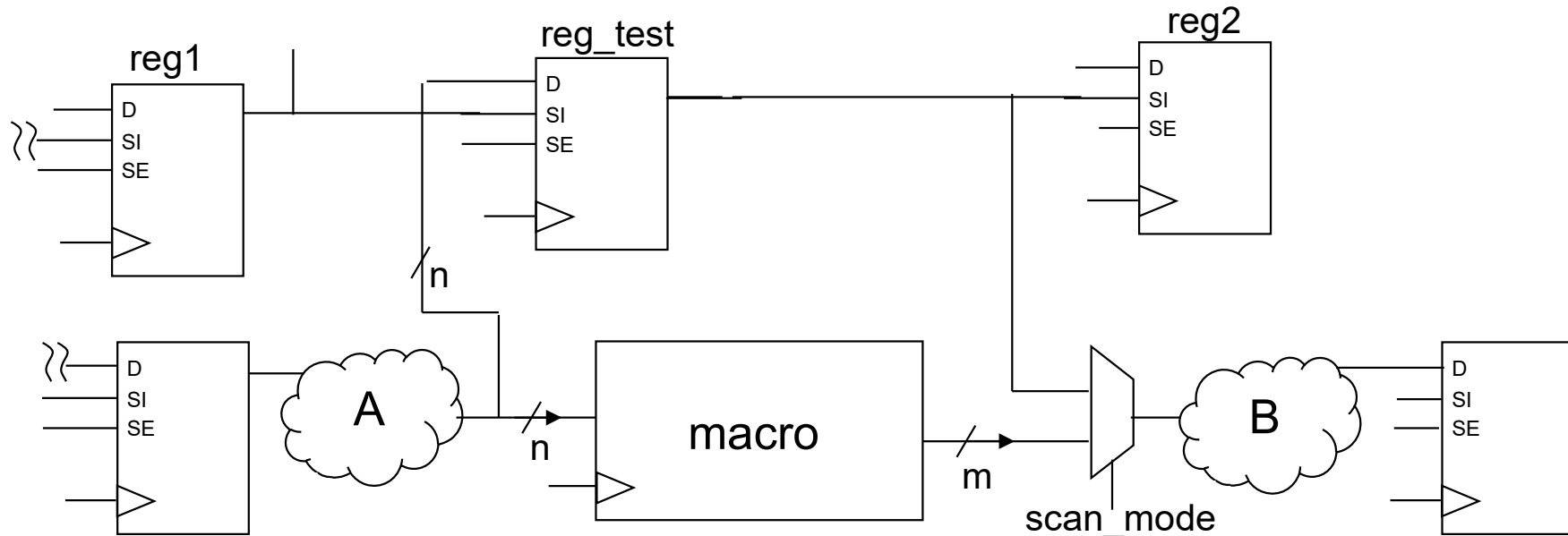
- Can use same FF for capture and control



- **reg_test**: capture & control FFs (inserted only for test)
 - capture outputs of “A” in capture mode
 - drive data through “B” in scan mode
- If $n \neq m$, will need additional capture-only or control-only flip-flops


Macro Bypass

 - Can eliminate common capture/control FF and simply bypass the macro in scan mode:




- In scan mode, data shifted into FF_A flows through A&B, and is captured in FF_B
 - macro bypassed
 - coverage obtained on A & B
 - If $n < m$, reuse inputs so that all outputs of macro are bypassed
 - if $n > m$, XOR inputs to reduce their count to “m”, and then bypass all macro outputs

XOR'ing extra inputs

 


- XOR gate preferred because output toggles any time an input toggles
 - makes it easier for ATPG tool to generate patterns
 - in 2-input NAND gate (for example), output does not toggle (remains “1”) when one input toggles, if the other input is “0”

Example: Embedded Memory

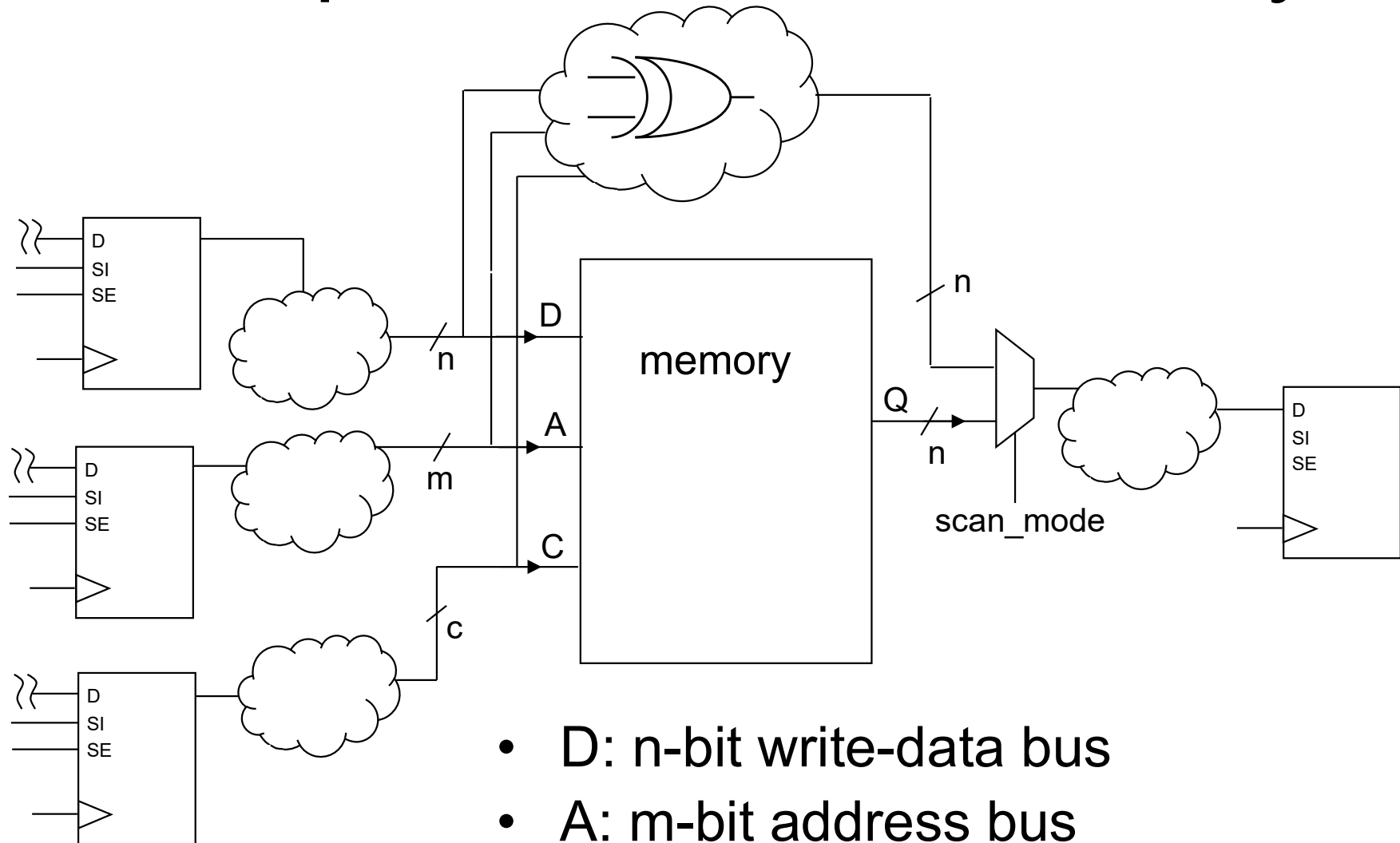

- D: n-bit write-data bus
- A: m-bit address bus
- C: c-bit control bus
- Q: n-bit read-data bus

Example: DAC & ADC

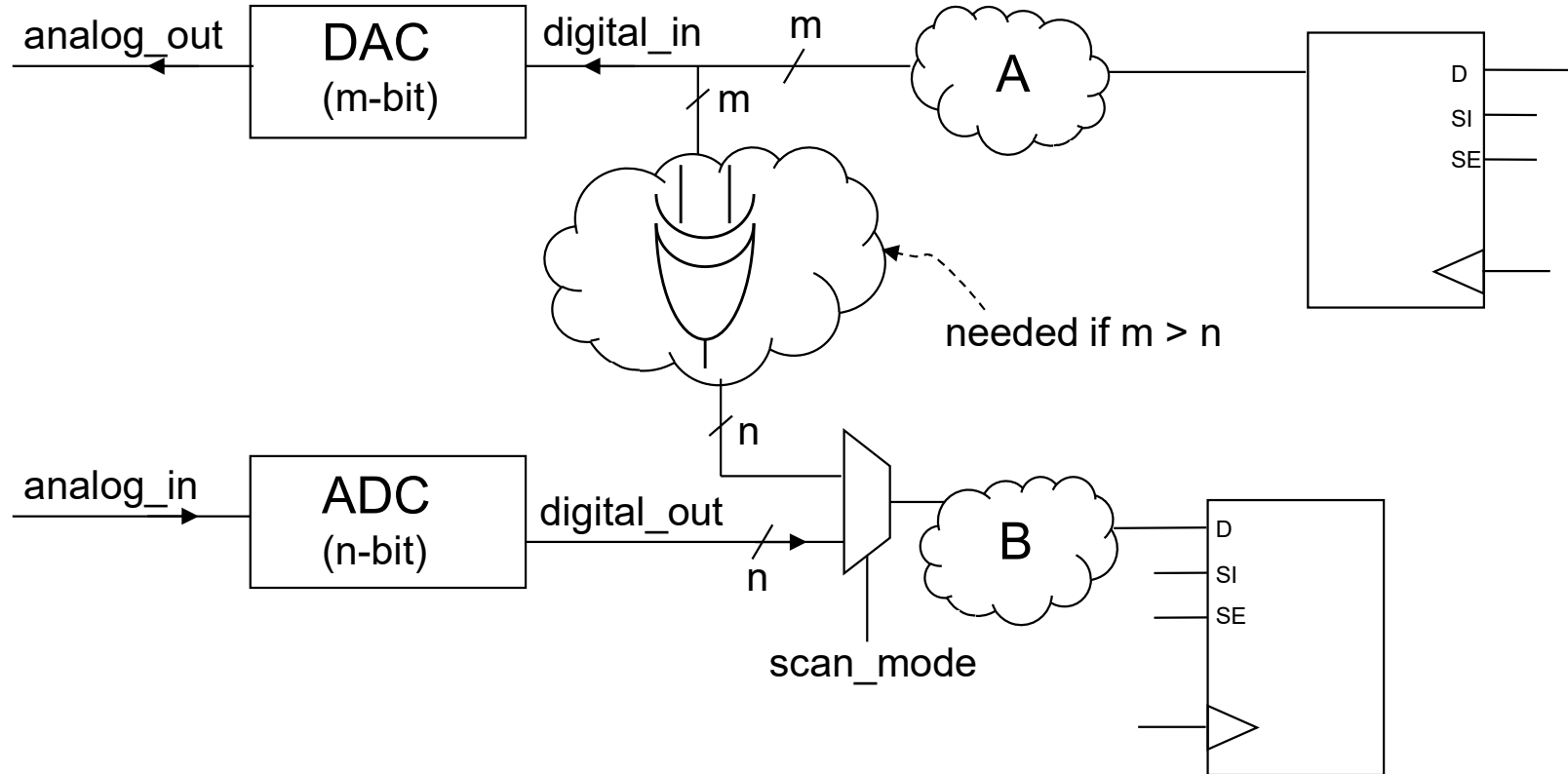

Scan Chain Balancing

- No. of shift cycles per pattern = length of longest scan chain
- Making all chains of equal length (or at least as equal as possible) reduces maximum scan chain length: this is called “scan chain balancing”

Tester Time & Cost


- Number of clock cycles required to fully populate a scan chain = number of flip-flops in the chain (“length” of scan chain)
- Test cost \propto time on tester
 - longer the length of the scan chain, the more it costs to test the chip with scan
- Test time for scan dominated by shift operation
 - capture takes one clock cycle, while shift can take hundreds or thousands of cycles. Ignoring capture cycle,
test time =

Tester Memory

- A tester has a fixed amount of memory in which the “test program” (test patterns in a tester-specific format) must be stored
- Required tester memory \propto (pattern count) \times (max. length of scan chain)
- If required memory exceeds tester memory, patterns have to be loaded and executed in chunks \Rightarrow large increase in tester time (and therefore test cost)


Scan Chain Balancing and Tester Memory

 - Max scan chain length is minimized if scan chains are balanced
 - scan chain balancing leads to optimal use of tester memory



Coverage vs. Pattern Count

 - Beyond certain count, additional patterns may make only a small incremental contribution to coverage
 - Can eliminate these patterns to reduce tester time and memory
 - ATPG software will generate such “fault grading” data



last 1000 patterns contribute
an additional coverage of
only 0.15%

“At-Speed” Scan

- Scan clocks are run at low frequency (compared to usual functional clocks) in conventional scan
 - less power consumption
 - fewer setup violations
 - “Stuck at” faults, which are manifested at any speed, can be detected with slow scan clocks
- Timing-related faults are not detected at conventional scan clock frequencies
 - Manifest only at high clock frequencies, going undetected at slow clock frequencies
 - transition faults (slow-to-rise, slow-to-fall)
 - path delay faults

“At Speed” Scan


- Circuit activity can be very high during shift, leading to excessive power consumption and IR-drop at high clock frequency

$$P = CV^2f_{\alpha}$$

- Biggest problem is meeting setup timing of the SE signal when it toggles between shift & capture cycles

SE Timing in At-Speed Test

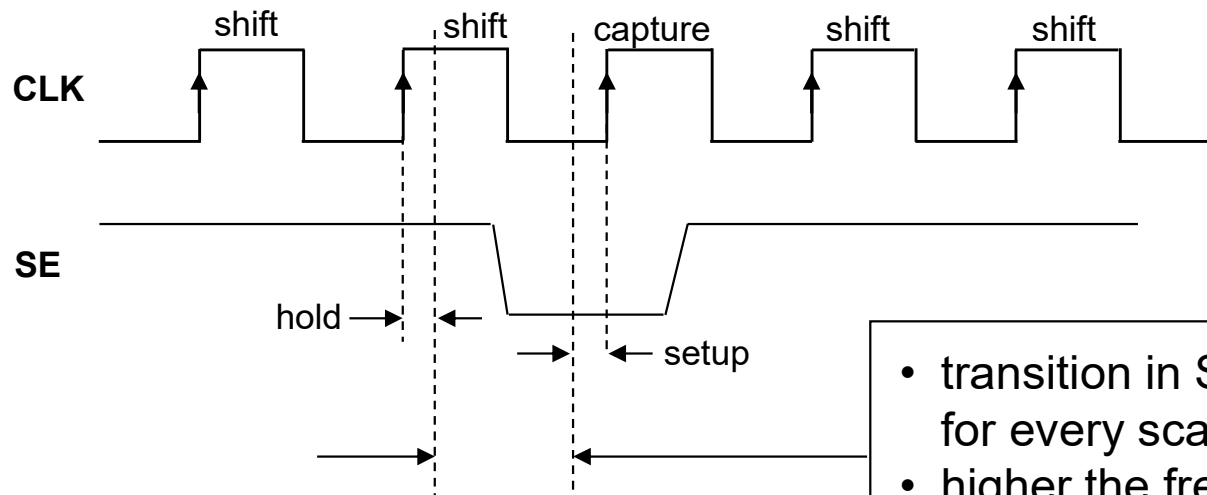
- SE signal goes to all scannable FFs
 - distributed in a similar way to the clock (i.e., as a “tree”)
- delay from SE source to FF (“insertion delay”) can be large (esp. to FFs distant from source)
- SE must meet setup & hold requirements at every FF
 - possible, but difficult when clock frequency is high



- transition in SE must fall within this window for every scannable FF in the netlist
- higher the frequency, narrower the window
⇒ more difficult to hit everywhere
 - clock skew shifts window location for different FFs

Doing At-Speed Test

 - One way to do at-speed testing is by using two capture pulses:
 - Capture pulses at high-speed
 - Shift cycles at low speed



- No setup requirements for SE at HF
- May need on-chip circuitry to generate pair of high-speed capture pulses when SE is low
- ATPG tool should be able to generate the right vectors
 - can target only minimum slack paths