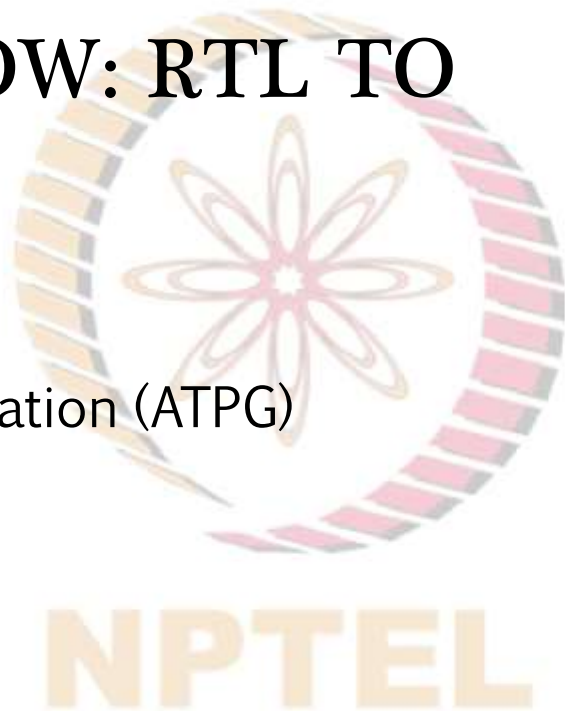


VLSI DESIGN FLOW: RTL TO GDS

Lecture 33


Automatic Test Pattern Generation (ATPG)



Sneh Saurabh
Electronics and Communications
Engineering
IIT Delhi

Lecture Plan

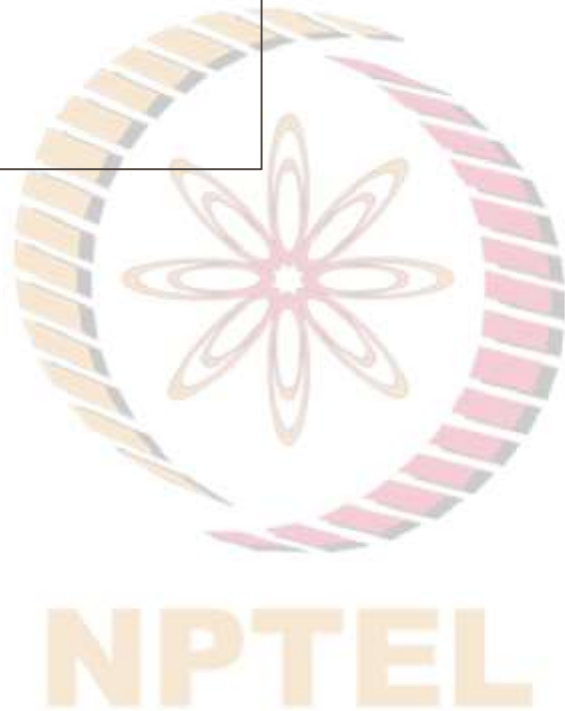- Terminologies
- General approach to ATPG
- Redundant Faults



Talking to a kitten ...

“... they always purr. ‘If they would only purr for “yes” and mew for “no,” or any rule of that sort’ she had said, ‘so that one could keep up a conversation!’

But how can you talk with a person if they always say the same thing?’

On this occasion the kitten only purred: and it was impossible to guess whether it meant ‘yes’ or ‘no’.”

—Lewis Carroll, *Through the Looking-Glass*, Chapter 12, 1871



Source:
<https://commons.wikimedia.org/wiki/File:LewisCarrollSelfPhoto.jpg> Lewis Carroll, Public domain, via Wikimedia Commons

ATPG: Objective, Challenges and Practical Solution

ATPG: Automatic Test Pattern Generator

- **Objective:** Generate test patterns (test vectors) that can be used to detect faults
- **Desired:** small set of test vectors that detect all faults considered for that circuit


Challenges

- For generalized sequential circuits, generating test vectors/sequences is very difficult
 - Reaching certain states may take exponential clock cycles
- Finding the test sequence that controls or observes an internal point in the circuit is runtime intensive

Practical Solution

- Sequential ATPG problem is transformed to Combinational ATPG problem by Scan Design Flow
- Combinational ATPG problem, though NP-complete, has efficient algorithms

ATPG: Terminologies

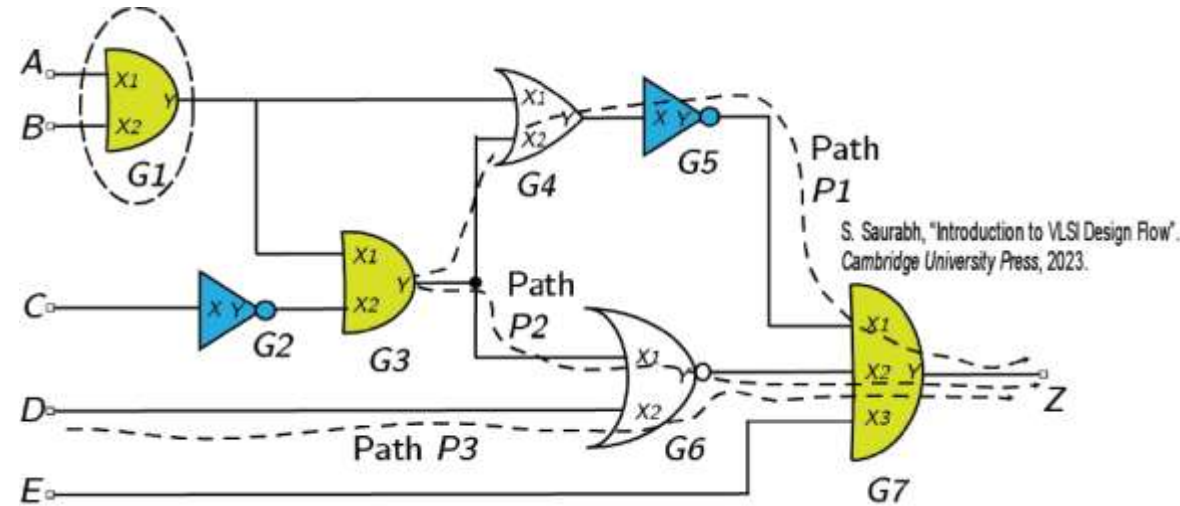

- **Path:** sequence of pins in topological order
- **On-path input** or **on-input:** for a given path, the input pins lying on that path
- **Side path inputs** or **side-inputs:** The input pins other than the on-inputs of the instances lying on that path

ATPG: Controlling/Non-controlling values

Controlling value of a multi-input gate

- Value that can be assigned to any input of the gate such that the output is known irrespective of values on other inputs.

Non-controlling value of a multi-input gate


- Value that can be assigned to any input of the gate such that the output is decided by the value on other inputs

Type of Gate	Controlling Value	Non-controlling value
AND	0	1
NAND	0	1
OR	1	0
NOR	1	0
XOR	Not defined	Any value


ATPG: General Approach

Path Sensitization Method

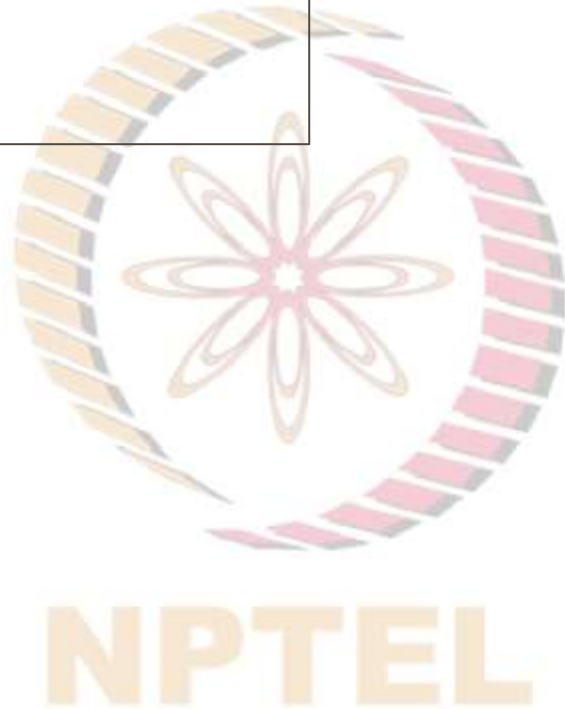- Fault Sensitization
- Fault Propagation
- Line Justification



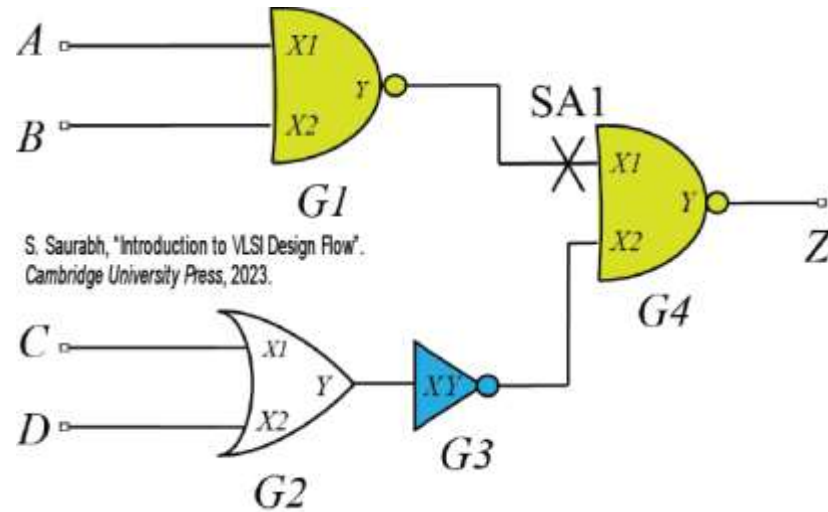ATPG: Illustration of Path Sensitization Method



Given: Stuck-at 1 at $G4/X1$

To Find: A test vector (value of A, B, C, D) which will be able to detect the existence of SA1 at $G4/X1$

Test Vector: (1,1,0,0)

- **Fault Sensitization:** Find the value at input ports that will set the value at the fault site **opposite** of the fault value

- Find A, B, C, D such that $G4/X1=0$ (A=1, B=1)


- **Fault Propagation:** For the path from the fault site to the output port, set the value of side-inputs to non-controlling inputs

- Set $G4/X2$ to non-controlling value ($G4/X2=1$)

- **Line Justification:** Find the value at input ports that will set the side-inputs as found in fault propagation

- Find A, B, C, D such that $G4/X2=1$ (C=0 D=0)

ATPG: Illustration of Backtracking

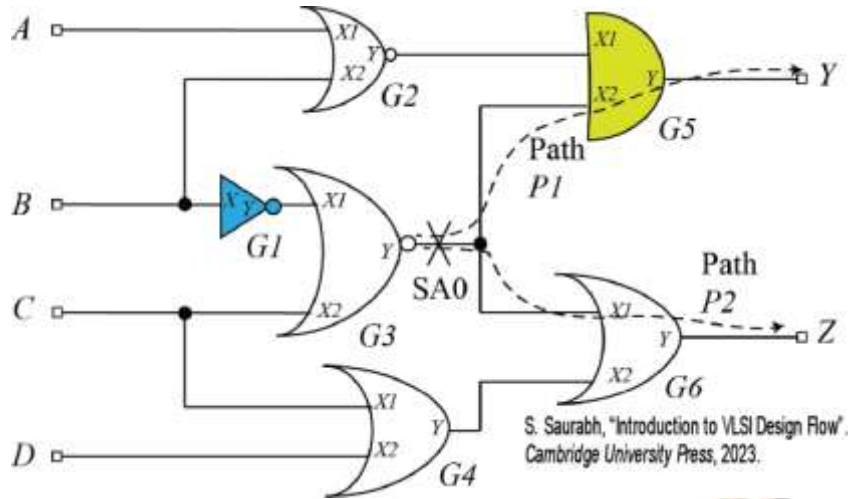


Given: Stuck-at 0 at $G3/Y$

To Find: A test vector to detect this fault.

Test Vector: (x,1,0,0)

- Fault Sensitization
 - Find A, B, C, D such that $G3/Y=1$ ($B=1, C=0$)
- Fault Propagation: **Path to Y**
 - Set $G5/X1$ to non-controlling value (i.e. 1)
- Line Justification: $A=0, B=0$
 - **$B=0$ is in conflict!**
 - Must be Backtracked
- Fault Propagation: **Path to Z**
 - Set $G6/X2$ to non-controlling value (i.e. 0)
- Line Justification: $C=0, D=0$

ATPG: Illustration of Redundant Fault

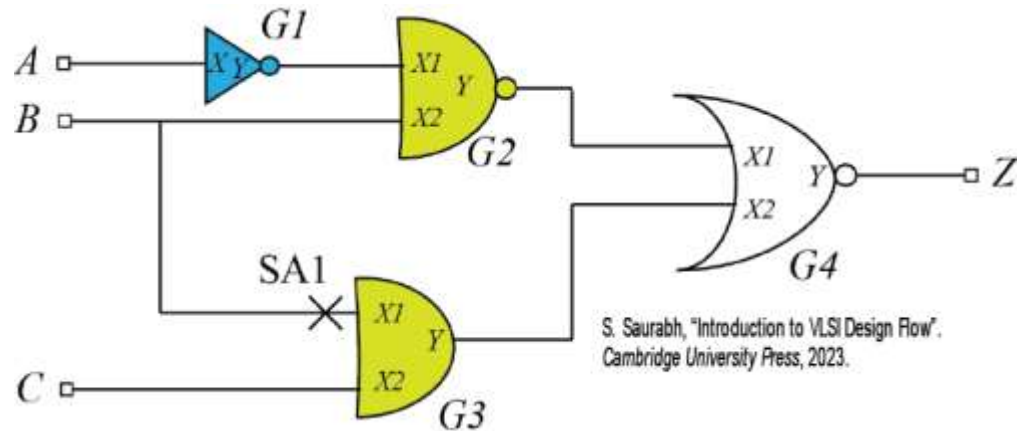

- Fault Sensitization
 - Find A, B, C such that $G3/X1=0$ ($B=0$)
- Fault Propagation:
 - For Propagation to Z: Set $G3.X2=1$ and $G4/X1=0$
- Line Justification:
 - $B=1$ is in conflict with earlier $B=0$



Given: Stuck-at 1 at pin $G3/X1$

To Find: A test vector to detect this fault

- No test vector exists to detect this fault
- This is known as *redundant fault*

ATPG: Redundant Fault based Optimization

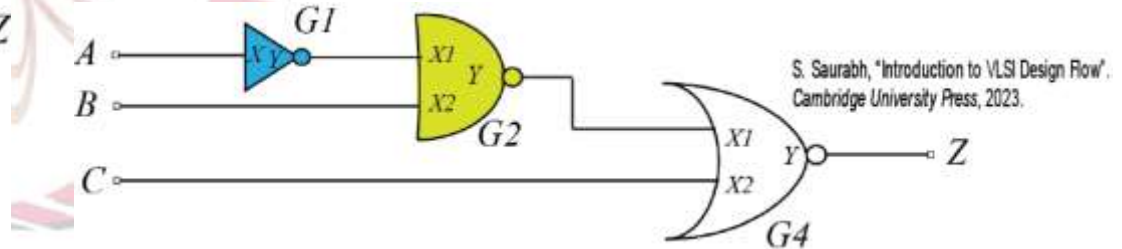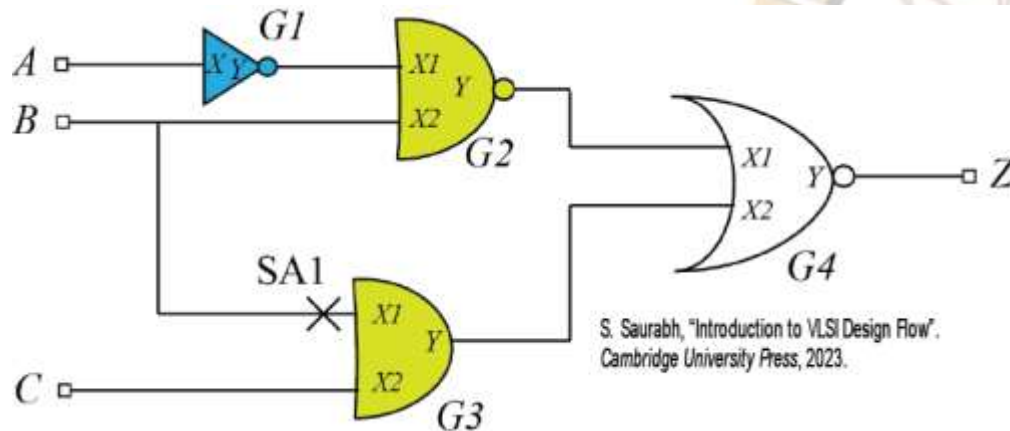- Redundant faults can be used to reduce the hardware
- Redundant fault means that the behavior of the circuit with/without fault is the same
- Assume that the fault site has constant 0/1 optimize out gates that are not required



- Assume that SA1 at $G3/X1$ is always present.
- $G3/X1=1$ implies that $G3/Y=C$

ATPG: Challenges and Solutions

Complications

- Primarily due to re-convergent fanouts
- Decisions required to be taken at a particular point
- Decision leads to implications
- Some decisions can be wrong (leading to conflicts in decisions)
 - Backtracking required

Backtracking Limit

- Too many backtrack => possible redundant fault
- User defined Backtrack Limit employed by tool
 - Example Backtrack Limit = 1000
 - Abort finding test vector when backtrack limit is hit, i.e. when 1000 times backtracking has been done

Algorithmic Advancements

- D-algorithm: Roth 1966
- PODEM (Path-oriented Decision Making): Prabhu Goel 1981
- FAN (Fanout-oriented) Algorithm: Fujiwara

References

- M. Bushnell and V. Agrawal, “Essentials of electronic testing for digital, memory and mixed-signal VLSI circuits”, *Springer Science & Business Media*, 2004.
- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

